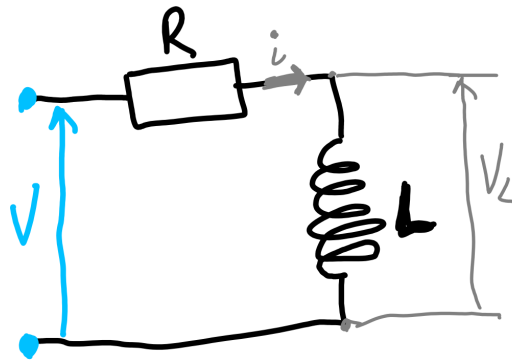


Applications of ODE: Inrush overcurrent in a linear inductor (I)

© 2025, Antonio Sala, Universitat Politècnica de València. All rights reserved.



Presentation in video: <https://personales.upv.es/asala/YT/V/LinrushlinEN.html>

*Python code there as well.

See also <https://youtu.be/x24545H5HdU?si=8KGq9tnQAULMkciZ> from other channel.

```
L=1; R=1.5;
```

Differential equation:

$$\frac{di}{dt} = \frac{1}{L} \cdot (V - R \cdot i)$$

Normalized form $\dot{x} = Ax + Bu$:

$$\frac{di}{dt} = \frac{-R}{L} \cdot i + \frac{1}{L} \cdot V$$

```
t_final=2.2;
syms t real
syms i(t)
omega=50*2*sym(pi); %50 Hz AC
ph0=0*pi/2; %initial phase (we'll play with it later on)
%ph0=-phaseI_ss;
V_peak=120;
V(t)=V_peak*sin(omega*t+ph0) %input voltage
```

```
v(t) = 120 sin(100 pi t)
```

```
vpa(V(t), 4)
```

```
ans = 120.0 sin(314.2 t)
```

Let us solve $\frac{di}{dt} = \frac{1}{L} \cdot (V - R \cdot i)$:

```
sol=dsolve( diff(i)==(V(t)-R*i(t))/L , i(0)==0) %ODE symbolic
solution
```

```
sol =
```

$$\frac{120 \left(\frac{3 \sin(100 \pi t)}{2} - 100 \pi \cos(100 \pi t) \right)}{10000 \pi^2 + \frac{9}{4}} + \frac{48000 \pi e^{-\frac{3t}{2}}}{40000 \pi^2 + 9}$$

```
vpa(sol,4)
```

```
ans = 0.001824 sin(314.2 t) - 0.382 cos(314.2 t) + 0.382 e-1.5 t
```


```
circuit_pole=-R/L %coefficient of the exponential
```

```
circuit_pole =  
-1.5000
```

```
t_settling=fzero(@(t) exp(circuit_pole*t)-0.05,0) % 5 percent  
settling time
```

```
t_settling =  
1.9972
```
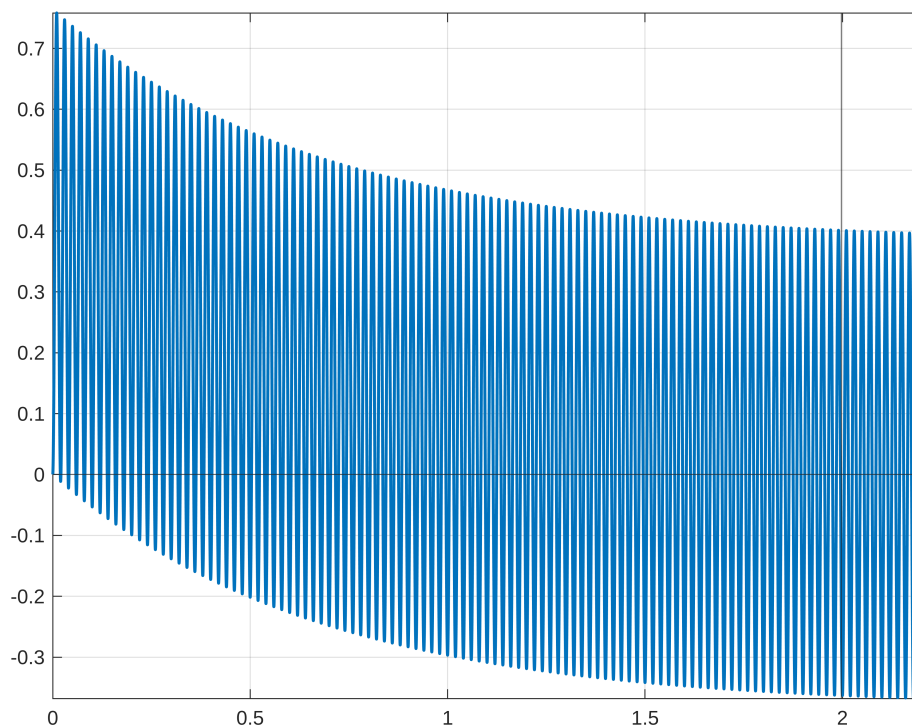
```
fplot(sol,[0 t_final],LineWidth=1.5), grid on, yline(0),  
xline(t_settling)
```




No resistor particular case

In this case $\frac{di}{dt} = \frac{1}{L} V$; hence $i(t) = i(0) + \frac{1}{L} \cdot \int_0^t V(\tau) d\tau$

```
syms tau real
i_noR=int(V(tau)/L,0,t)+0;
vpa(i_noR,4)
```

```
ans = 0.7639 sin(157.1 t)^2
```
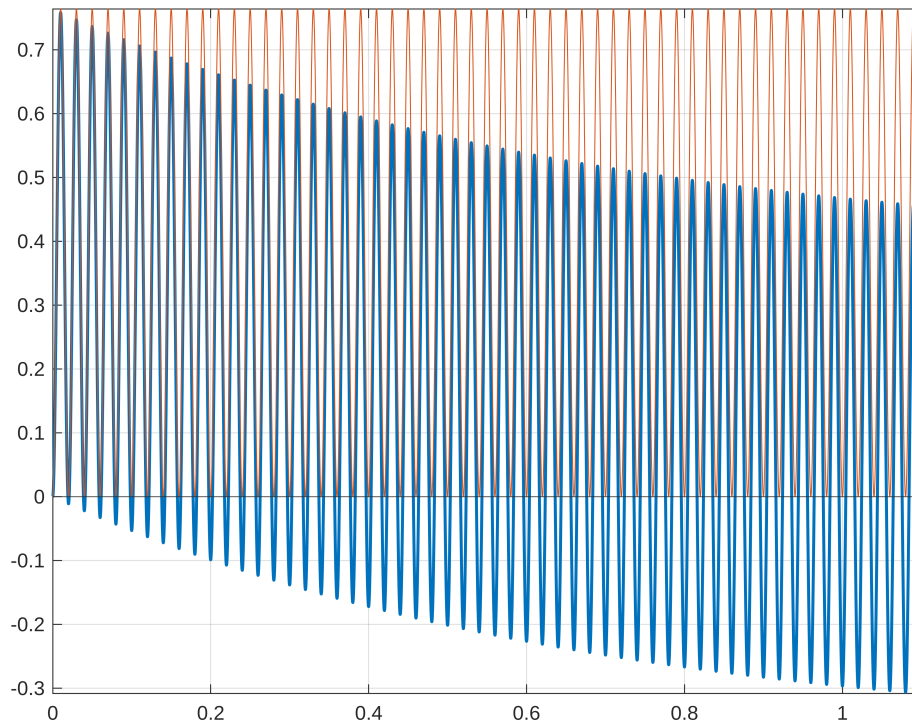
```
figure()
fplot(sol,[0 t_final/2], LineWidth=1.5), hold on
fplot(i_noR,[0 t_final/2]), hold off
grid on, yline(0)
```



Particular case 2: steady state sinusoidal regime

```
Z=R+L*omega*1j %impedance
```

```
Z =  
 $\frac{3}{2} + 100\pi i$ 
```

```
amplI_ss=abs(1/Z)*V_peak; %Current amplitude  
eval(amplI_ss)
```

```
ans =  
0.3820
```


```
phaseI_ss=angle(1/Z);  
eval(phaseI_ss)*180/pi
```

```
ans =  
-89.7264
```

```
I_ss=simplify(amplI_ss*sin(omega*t+phaseI_ss+ph0),120);
vpa(I_ss,4)
```

```
ans = -0.382 sin(1.566 - 314.2 t)
```
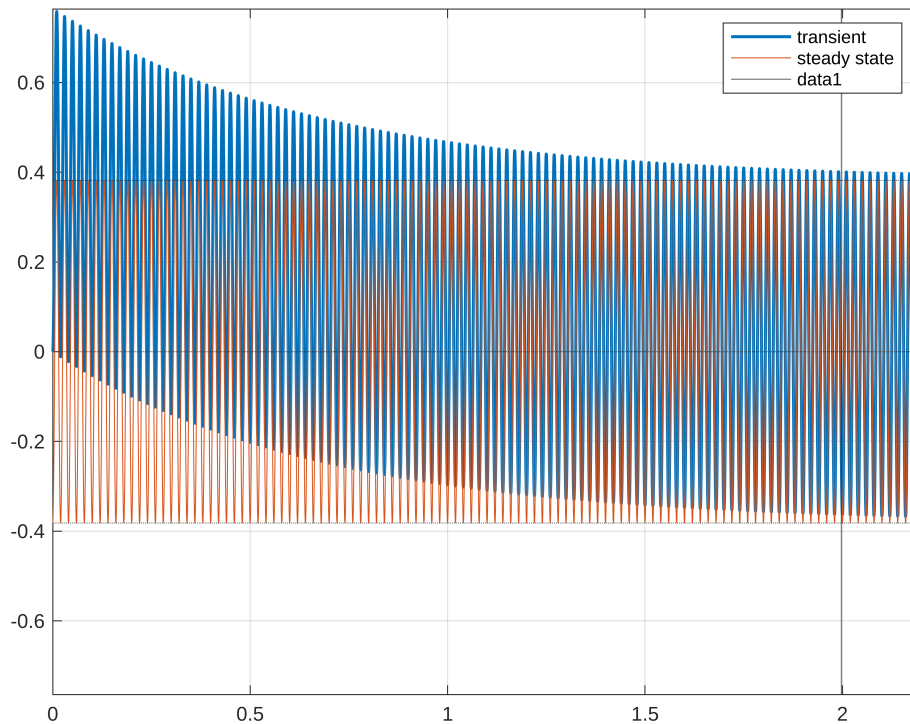
```
figure()
fplot(sol,[0 t_final],LineWidth=1.5), hold on
fplot(I_ss,[0 t_final]), hold off
yline([-2 -1 0 1 2]'*eval(amplI_ss),'::'), grid on
legend("transient", "steady state",
Location="best"),xline(t_settling)
```



Conclusions

Initial response close to "no resistor" case, which has a non-vanishing DC component.

- If $V(0) = 0$, we have twice initial current to that of steady state from impedance

computations (2x inrush current); it takes $\approx 3 \frac{L}{R}$ seconds to vanish.

- If phase of voltage equal to that of conductance (inverse impedance) then we start "spot on" the steady-state sinusoid, inrush current avoided. It is close to 90° for a heavily inductive load.

- **Inrush current** in real transformers may be much higher (6x or more), due to magnetic saturation (in another video). Harmonics (non-sinusoidal waveforms) also appear in such a

case. Fuse ratings, energization timing, serial resistance, etc. must be considered with care in, say, high-power transformer startup.